

5.4

**5.4** An NMOS transistor that is operated with a small  $v_{DS}$  is found to exhibit a resistance  $r_{DS}$ . By what factor will  $r_{DS}$  change in each of the following situations?

- (a)  $V_{OV}$  is doubled.
- (b) The device is replaced with another fabricated in the same technology but with double the width.
- (c) The device is replaced with another fabricated in the same technology but with both the width and length doubled.
- (d) The device is replaced with another fabricated in a more advanced technology for which the oxide thickness is halved and similarly for  $W$  and  $L$  (assume  $\mu_n$  remains unchanged).

**(a)**

$$r_{DS} = \frac{1}{g_{DS}}$$

$$g_{DS} = k_n v_{OV}$$

$$\Rightarrow r_{DS} = \frac{1}{k_n v_{OV}}$$

$$\frac{r_{DS_{new}}}{r_{DS}} = \frac{1/(k_n 2v_{OV})}{1/(k_n v_{OV})} = \frac{1}{2}$$

$r_{DS}$  is halved.

**(b)**

The device width is proportional to the MOSFET transconductance parameter,  $k_n$ . So,

$$k_{n_{new}} = 2k_n.$$

As in (a),

$$\frac{r_{DS_{new}}}{r_{DS}} = \frac{1/(2k_n v_{OV})}{1/(k_n v_{OV})} = \frac{1}{2}.$$

$r_{DS}$  is halved.

**(c)**

Since the aspect ratio stays the same, the MOSFET transconductance parameter, stays the same. Therefore,

$r_{DS}$  stays the same.

**(d)**

As per (c), the aspect ratio stays the same and hence we will disregard the width,  $W$ , and length,  $L$ , for the total effect on  $r_{DS}$ .

The thickness of the oxide layer will have an effect on  $r_{DS}$ . The MOSFET transconductance parameter is proportional to the process transconductance parameter. The thickness of the oxide layer is inversely proportional to the process transconductance parameter. So, the MOSFET transconductance parameter,  $k_n$ , is inversely proportional to the thickness of the oxide layer,  $t_{ox}$ . We can relate this proportionality to  $r_{DS}$ :

$$k_n \propto t_{ox}^{-1}$$

$$r_{DS} \propto k_n^{-1}$$

$$\Rightarrow r_{DS} \propto t_{ox}.$$

Since  $t_{ox}$  is halved,  $r_{DS}$  is halved.

5.8

**5.8** Consider an NMOS transistor operating in the triode region with an overdrive voltage  $V_{OV}$ . Find an expression for the incremental resistance

$$r_{ds} \equiv 1 / \left. \frac{\partial i_D}{\partial v_{DS}} \right|_{v_{DS}=V_{DS}}$$

Give the values of  $r_{ds}$  in terms of  $k_n$  and  $V_{OV}$  for  $V_{DS} = 0$ ,  $0.2V_{OV}$ ,  $0.5V_{OV}$ ,  $0.8V_{OV}$ , and  $V_{OV}$ .

If  $V_{DS} \ll V_{OV}$ , then,

$$i_D = k_n V_{OV} V_{DS}$$

However, as  $V_{DS}$  rises,

$$i_D = k_n \left( V_{OV} - \frac{1}{2} V_{DS} \right) V_{DS}$$

where  $V_{OV} - \frac{1}{2} V_{DS}$  replaces  $V_O$  due to tapering from an increase in holes at the drain.

So,

$$r_{DS} = \left[ \frac{\delta i_D}{\delta v_{DS}} \right]^{-1}$$

becomes,

$$\begin{aligned} r_{DS} &= \left[ \frac{1}{\delta v_{DS}} \left( k_n \left( V_{OV} - \frac{1}{2} V_{DS} \right) V_{DS} \right) \right]^{-1} \\ &= \left[ k_n \left( V_{OV} \frac{1}{\delta v_{DS}} V_{DS} - \frac{1}{2} \frac{1}{\delta v_{DS}} V_{DS}^2 \right) \right]^{-1} \\ &= [k_n (V_{OV} - V_{DS})]^{-1} \end{aligned}$$

**case  $V_{DS} = 0$ :**

$$r_{DS} = \frac{1}{k_n V_{OV}}$$

**case  $V_{DS} = 0.2V_{OV}$ :**

$$r_{DS} = \frac{1}{k_n \cdot 0.8V_{OV}}$$

**case  $V_{DS} = 0.5V_{OV}$ :**

$$r_{DS} = \frac{1}{k_n \cdot 0.5V_{OV}}$$

**case  $V_{DS} = 0.8V_{OV}$ :**

$$r_{DS} = \frac{1}{k_n \cdot 0.2V_{OV}}$$

**case  $V_{DS} = V_{OV}$ :**

$$r_{DS} = \infty$$

5.24


**5.24** When the drain and gate of a MOSFET are connected together, a two-terminal device known as a “diode-connected transistor” results. Figure P5.24 shows such devices obtained from MOS transistors of both polarities. Show that

(a) the  $i$ - $v$  relationship is given by

$$i = \frac{1}{2} k' \frac{W}{L} (v - |V_t|)^2$$

(b) the incremental resistance  $r$  for a device biased to operate at  $v = |V_t| + V_{ov}$  is given by

$$r \equiv 1 / \left[ \frac{\partial i}{\partial v} \right] = 1 / \left( k' \frac{W}{L} V_{ov} \right)$$

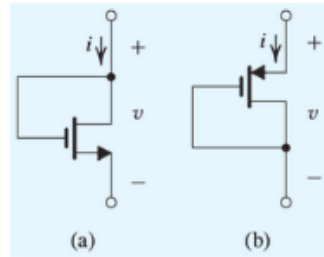

**Fig. P5.24**

**(a)**

Since  $V_{DS} = V_{OV}$ , the NMOS is saturated and the current through the transistor is,

$$i = \frac{1}{2} k_n (v - |V_t|)^2$$


where  $i = i_{DS}$  and  $v = V_{GS} = V_{DS}$ .

**(b)**

$$\begin{aligned} r &= \left[ \frac{\delta i}{\delta v} \right]^{-1} \\ &= \frac{1}{2k' \frac{W}{L} (v - V_t)} \\ &= \frac{1}{k'_n \frac{W}{L} V_{OV}} \end{aligned}$$

5.28

**5.28** The NMOS transistor in Fig. P5.28 has  $V_t = 0.4$  V and  $k'_n(W/L) = 1$  mA/V<sup>2</sup>. Sketch and clearly label  $i_D$  versus  $v_G$  with  $v_G$  varying in the range 0 to +1.8 V. Give equations for the various portions of the resulting graph.

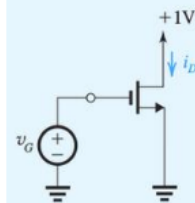

**Figure P5.28**

graph  $i_D$  vs  $V_G$

 


Figure 1: Note that  $k_n = k'_n \frac{W}{L} = 1\text{mA}$  and represents the MOSFET transconductance parameter.

**case**  $0V \leq V_G \leq V_t = 0.4V$

The NMOS is off since  $V_G < V_t$ . So,

$$i_D = 0\text{mA}$$

**case**  $V_t = 0.4V < V_G \leq V_t + V_{DS} = 1.4V$

The NMOS is saturated since  $V_{DS} \geq V_G - V_t$ .

$$i_D = \frac{1}{2} k_n V_{OV}^2 = \frac{1}{2} \cdot 1\text{mA} \cdot (V_G - 0.4V)^2$$

**case**  $V_t + V_{DS} = 1.4V \leq V_G \leq 1.8V$

The NMOS is operating in the triode region.

$$i_D = k_n \left( V_{OV} - \frac{1}{2} V_{DS} \right) V_{DS} = 1\text{mA} \cdot (V_G - 0.9)$$

5.39

**5.39** A  $p$ -channel transistor for which  $|V_t| = 0.8\text{ V}$  and  $|V_A| = 40\text{ V}$  operates in saturation with  $|v_{GS}| = 3\text{ V}$ ,  $|v_{DS}| = 4\text{ V}$ , and  $i_D = 3\text{ mA}$ . Find corresponding signed values for  $v_{GS}$ ,  $v_{SD}$ ,  $V_t$ ,  $V_A$ ,  $\lambda$ , and  $k'_p(W/L)$ .

$$v_{GS} = -3V$$

$$v_{SG} = 3V$$

$$v_{DS} = -4V$$

$$v_{SD} = 4V$$

$$V_t = -0.8V$$

$$V_A = -40V$$

$$\lambda = \frac{1}{V_A} = -25\text{mV}$$

$$i_D = \frac{1}{2}k_p(V_{GS} - V_t)^2(1 + \lambda v_{DS})$$

$$3\text{mA} = \frac{1}{2}k_p(-3 + 0.8)^2(1 + .025 \cdot 4)$$

$$\rightarrow k_p = 1.13\text{mA/V}^2$$

5.44

**D 5.44** Design the circuit of Fig. P5.44 to establish a drain current of 0.1 mA and a drain voltage of +0.3 V. The MOSFET has  $V_t = 0.5$  V,  $\mu_n C_{ox} = 400 \mu\text{A/V}^2$ ,  $L = 0.4 \mu\text{m}$ , and  $W = 5 \mu\text{m}$ . Specify the required values for  $R_S$  and  $R_D$ .

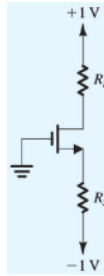


Fig. P5.44

**find**  $R_D$

We know the voltage drop across  $R_D$  and the branch current. So,

$$R_D = \frac{1\text{V} - 0.3\text{V}}{0.1\text{mA}} = \boxed{7\text{k}\Omega}$$

**find**  $R_S$

We need to know the voltage at the NMOS source,  $V_S$ , to figure out the voltage drop across  $R_S$ .

$$k_n = \mu_n C_{OX} \frac{W}{L} = 0.4\text{mA/V}^2 \cdot \frac{5\mu\text{m}}{0.4\mu\text{m}} = 5\text{mA/V}^2$$

Since  $V_D > V_G$ , the NMOS is saturated. So,

$$i_D = \frac{1}{2}k_n v_{OV}^2$$

$$0.1\text{mA} = \frac{1}{2} \cdot 5\text{mA/V}^2 \cdot v_{OV}^2$$

$$v_{OV} = 0.2\text{V}$$


$$V_{GS} = v_{OV} + V_t = 0.2 + 0.5 = 0.7\text{V}$$

$$V_S = -0.7\text{V}$$

$$R_S = \frac{V_S - (-1\text{V})}{i_D} = \frac{-0.7 + 1}{0.1\text{mA}} = \boxed{3\text{k}\Omega}$$

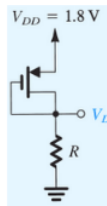5.49

**D 5.49** The PMOS transistor in the circuit of Fig. P5.49 has  $V_t = -0.5$  V,  $\mu_p C_{ox} = 100 \mu\text{A/V}^2$ ,  $L = 0.18 \mu\text{m}$ , and  $\lambda = 0$ . Find the values required for  $W$  and  $R$  in order to establish a drain current of  $180 \mu\text{A}$  and a voltage  $V_D$  of 1 V.



$$R = \frac{V_D}{i_D} = \frac{1V}{.18mA} = \boxed{5.6k\Omega}$$

Since  $V_D = V_G$ , the PMOS is saturated.

$$i_D = \frac{1}{2} k'_p \frac{W}{L} (v_{SG} - |V_t|)^2$$


$$v_{SG} = V_{DD} - V_D = 0.8V$$

$$.18mA = \frac{1}{2} \cdot .1mA/V^2 \cdot \frac{W}{.18\mu m} \cdot (0.8V - 0.5V)^2$$

$$\rightarrow \boxed{W = 7.2\mu m}$$

 5.51

**D 5.51** The NMOS transistors in the circuit of Fig. P5.51 have  $V_t = 0.5V$ ,  $\mu_n C_{ox} = 90 \mu A/V^2$ ,  $\lambda = 0$ , and  $L_1 = L_2 = L_3 = 0.5 \mu m$ . Find the required values of gate width for each of  $Q_1$ ,  $Q_2$ , and  $Q_3$  to obtain the voltage and current values indicated.



$$i_D: 90 \mu A$$

Since  $V_D = V_G$  for each NMOS, each NMOS is saturated. This gives,

$$i_D = \frac{1}{2} k_n' \frac{W}{L} V_{ov}^2$$

$$90 \mu A = \frac{1}{2} \cdot 90 \mu A/V^2 \cdot \frac{W}{0.5 \mu m} V_{ov}^2$$

For each  $Q$ ,

$$W = \frac{I}{V_{ov}^2} \quad \text{where } V_{ov} = V_{DS} - V_t$$

$$W = \frac{1}{(V_{DS} - 0.5)^2}$$

Case  $Q_3$  ( $V_{DS} = 1$ ):

$$\boxed{W_3 = 4 \mu m}$$

Case  $Q_2$  ( $V_{DS} = 0.7$ ):

$$\boxed{W_2 = 25 \mu m}$$

Case  $Q_1$  ( $V_{DS} = 0.8$ ):

$$\boxed{W_1 = 11.1 \mu m}$$

5.56

5.56 For each of the circuits in Fig. P5.56, find the labeled node voltages. For all transistors,  $k'_n(W/L) = 0.5 \text{ mA/V}^2$ ,  $V_t = 0.8 \text{ V}$ , and  $\lambda = 0$ .

$$k_n = 0.5 \text{ mA/V}^2, \text{ let } V = V_{GS} = V_{DS}$$

(a)  $V_D = V_G$ , so NMOS is saturated.

$$i_D = \frac{1}{2} k_n (V - V_t)^2$$

$$R = \frac{5 - V}{i_D}$$

$$\frac{5 - V}{2.2 \text{ k}\Omega} = \frac{1}{2} \cdot 0.5 \text{ mA/V}^2 \cdot (V - 0.8)^2$$

$$9.09 - 1.82V = V^2 - 1.6V + 0.64$$

$$V^2 + 0.22V - 8.45 = 0$$

from python,

$$V = 2.8 \text{ [V]}$$

(b)  $V_D > V_G$ , so NMOS is saturated.

$$i_D = \frac{1}{2} k_n (V_{GS} - V_t)^2 \quad V_{GS} = 0 - V_S = -V_S$$

$$R = \frac{V_S + 5}{i_D} \rightarrow i_D = \frac{V_S + 5}{400 \text{ k}\Omega}$$

$$\frac{V_S + 5}{400 \text{ k}\Omega} = \frac{1}{2} \cdot 0.5 \text{ mA/V}^2 \cdot (-V_S - 0.8)^2$$

$$0.01V_S + 0.06 = (-V_S - 0.8)^2$$


$$= V_S^2 + 1.6V_S + 0.64$$

$$V_S^2 + 1.59V_S + 0.59 = 0$$

$$V_S = -1, -0.59$$

$V_{GS} = 0.59 < V_t$   
BAD ROOT

$$V_S = -1 \text{ [V]}$$

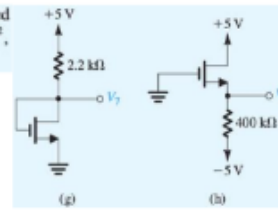

5.58