

7.30

**7.30** For the NMOS amplifier in Fig. P7.30, replace the transistor with its T equivalent circuit, assuming  $\lambda = 0$ . Derive expressions for the voltage gains  $v_s/v_i$  and  $v_d/v_i$ .


 


Fig. P7.30

 

$$i_D = g_m v_{gs}$$

$$v_i = i_D \left( \frac{1}{g_m} + R_S \right)$$

$$v_s = i_D R_S$$

$$v_D = -i_D R_D \quad \therefore \frac{0 - v_D}{R_D} = i_D$$


$$\therefore \frac{v_s}{v_i} = \frac{i_D R_S}{i_D \left( \frac{1}{g_m} + R_S \right)} = \frac{R_S}{\frac{1}{g_m} + R_S} = \frac{1}{\frac{1}{g_m R_S} + 1}$$

$$\therefore \frac{v_D}{v_i} = \frac{-i_D R_D}{i_D \left( \frac{1}{g_m} + R_S \right)} = -\frac{R_D}{R_S} \frac{1}{\frac{1}{g_m R_S} + 1}$$

 7.33

**\*7.33** Figure P7.33 shows a discrete-circuit amplifier. The input signal  $v_{sig}$  is coupled to the gate through a very large capacitor (shown as infinite). The transistor source is connected to ground at signal frequencies via a very large capacitor (shown as infinite). The output voltage signal that develops at the drain is coupled to a load resistance via a very large capacitor (shown as infinite). All capacitors behave as short circuits for signals and as open circuits for dc.

- If the transistor has  $V_t = 1$  V, and  $k_n = 4$  mA/V<sup>2</sup>, verify that the bias circuit establishes  $V_{GS} = 1.5$  V,  $I_D = 0.5$  mA, and  $V_D = +7.0$  V. That is, assume these values, and verify that they are consistent with the values of the circuit components and the device parameters.
- Find  $g_m$  and  $r_o$  if  $V_A = 100$  V.
- Draw a complete small-signal equivalent circuit for the amplifier, assuming all capacitors behave as short circuits at signal frequencies.
- Find  $R_{in}$ ,  $v_{gs}/v_{sig}$ ,  $v_o/v_{gs}$ , and  $v_o/v_{sig}$ .



②

$$V_{ov} = V_{GS} - V_t = 1.5 - 1.0 = 0.5 \text{ V}$$

Since  $V_{DS} \geq V_{ov}$ , the NMOS is saturated.


$$I_D = \frac{1}{2} K_n V_{ov}^2 \rightarrow 0.5 = \frac{1}{2} \cdot 4 \cdot 0.5^2 = 0.5.$$

↑  
VERIFIED

(b)

$$r_o = \frac{|V_A|}{I_D} = \frac{100V}{0.5mA} = 200k\Omega$$
 
$$g_m = \sqrt{2k_n I_D} = \sqrt{2 \cdot 4 \cdot 0.5} = 2mS$$



(d)

$$R_{in} = R_G = 3.33M\Omega$$

$$V_{gs} = V_{sig} \frac{R_G}{R_G + R_{sig}} \Rightarrow \frac{V_{gs}}{V_{sig}} = \frac{R_G}{R_G + R_{sig}} = 0.94$$

$$\frac{V_o}{V_{gs}} = -g_m (r_o || 16k || 16k) = -15.4$$

$$\frac{V_o}{V_{sig}} = \frac{V_o}{V_{gs}} \cdot \frac{V_{gs}}{V_{sig}} = -15.4 \cdot 0.94 = -14.48$$

7.121

**D \*7.121** The MOSFET in the circuit of Fig. P7.121 has  $V_t = 0.8V$ ,  $k_n = 5mA/V^2$ , and  $V_A = 40V$ .

- Find the values of  $R_S$ ,  $R_D$ , and  $R_G$  so that  $I_D = 0.4mA$ , the largest possible value for  $R_D$  is used while a maximum signal swing at the drain of  $\pm 0.8V$  is possible, and the input resistance at the gate is  $10M\Omega$ . Neglect the Early effect.
- Find the values of  $g_m$  and  $r_o$  at the bias point.
- If terminal Z is grounded, terminal X is connected to a signal source having a resistance of  $1M\Omega$ , and terminal Y is connected to a load resistance of  $10k\Omega$ , find the voltage gain from signal source to load.
- If terminal Y is grounded, find the voltage gain from X to Z with Z open-circuited. What is the output resistance of the source follower?